

## Nonlinear Modeling

- Nonlinear problems are difficult to solve
- The diode is a nonlinear device
- Picewise linear models can simplifying the solution of non linear circuits problems.

Lecture #2

## The purpose of modeling

- Nonlinear problems are much more difficult than linear ones. These problems could be impossible to solve manually and could require huge amount of time if solved on a computer.
- One possible solution of the above mentioned problem is to approximate the nonlinear relationship with a model that has a linear relationship.
- The trust of nonlinear modeling is direct towards this end.
- *The modeling not only simplifies the solution, it also allows the designer to understand how the circuit behaves. Modeling often increases the conceptual understanding of the circuit operation.*

Lecture #2

## Demonstration of the difficulty in solving nonlinear problems

- Consider a linear circuit (a) and nonlinear circuit (b). *Determine I and  $V_{out}$ ?*

• *Solution: In circuit (a):*

By simple ohm's law we can find current I as,

$$I = V_1 / R_1 + R_2 = 6 / (200 + 300) = 0.012A$$

The output voltage is then

$$V_{out} = IR_2 = 0.012 \times 300 = 3.6V$$


*Circuit (b):*

The current I can be determine by using diode equation as


$$I = I_s (e^{qV/kT} - 1) = 10^{-10} (e^{V_{out}/0.026} - 1)$$

*There is no close form solution of the above equation.*

Lecture #2

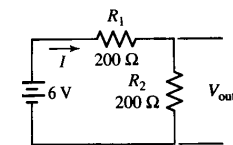

(a)

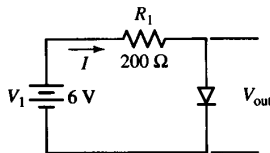

(b)

## Demonstration of the difficulty in solving nonlinear problems (cont.)

In order to determine  $V_{out}$  we have to solve another equation which can be written as by Kirchoff's law,

$$V_1 = IR_1 + V_{out}$$


$$\Rightarrow V_1 = 200 \times 10^{-8} (e^{V_{out}/0.026} - 1) + V_{out}$$

Again, there is no close form solution of the above equation.

Perhaps the quickest method for solving this problems is a *trial and error iterative method*.

If we guess many time, finally we will be able to show that, when  $V_{out} = 0.505215 \sim 0.5V$ , the right side of the above equation is **5.99V**, which is essentially equal to the value of the left side of the equation.

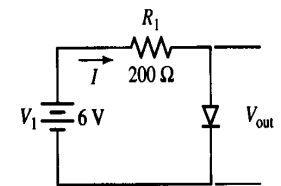Finally,  $I = 0.02747 \approx 0.027A$ . Lecture #2



(b)

## Possible model of the problem (constant voltage drop model)

- One possible model for the forward bias diode is a simple 0.6V voltage source.
- When this model replaces the diode, the circuit appear as shown in the figure and is very easy to analyze.
- For this circuit the current is calculated to be
- $I = (V_1 - 0.6) / 200 = 0.027 \text{ A}$
- And the  $V_{out} = 0.6 \text{ V}$
- These values compare well to the results calculated from the exact equations, but much easier to obtained.
- The above example demonstrate that how model simplifies the solution.

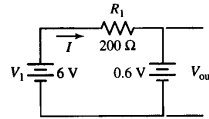


Figure 5.12  
The circuit of Fig. 5.11 with a simplified diode model.

Lecture #2

## A load line approach


- An alternate and more traditional graphical method to analyze a circuit containing a nonlinear element is that of using a load line.
- The load line can yield accurate results and used extensively in the evaluation of the electronic circuits.

Lecture #2

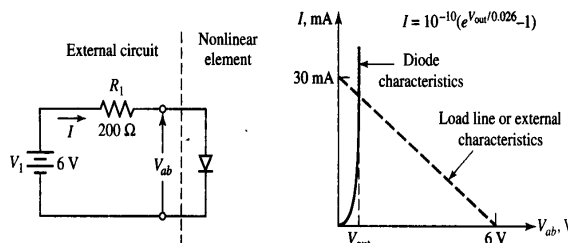
## Load line analysis

- In this approach the series circuit shown here can be split into a nonlinear element and the remaining external circuit.

$$\text{Load line equation: } V_{ab} = V_1 - IR_1$$




## Ideal diode model

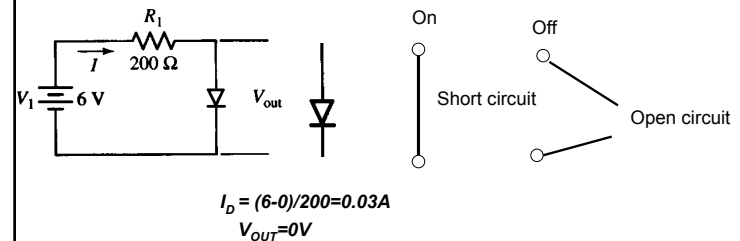


Lecture #2
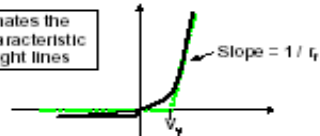
### Piecewise Linear Diode Model

Approximates the diode characteristic with straight lines



Forward bias

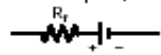

Simplified to before if  $R_f = 0$

Reverse bias



Lecture #2

### Conductor-to-Semiconductor Contact

- Must have some way of making electrical connections to semiconductors.
- If metal (Al, Pt, Au, Ag, Cu, etc.) deposited on clean semiconductor surface (Ge, Si, GaAs, etc.), the resulting contact:

- ◆ Rectifying
- ◆ Ohmic

### Metal-to-Semiconductor Contacts

- With contact between metal and semiconductor (let's assume Si),
  - ◆ Some path exists for electron flow from one material to the other.

Lecture #2

### Metal-to-Semiconductor Contacts

- At the contact, the energy level of electrons within both materials must be the same.
  - ◆ This energy level is also termed the "Fermi" level.
- To equalize energy, momentary movement of electrons from silicon and metal and vice versa.
  - ◆ Flow equalization depends on the metal type and the doping of silicon.

## Rectifying Contacts

- Consider an n-type semiconductor.
- Semiconductor doping level can result in fewer mobile electrons near the metal-silicon interface
- Thus, donor impurities (atoms) exist that do not have mobile electrons nearby to compensate their positive charge.

LECTURE 72

## Other Diode Types

- Conductor-to-Semiconductor Contacts
  - ◆ Schottky Diodes
- Junction Capacitance
  - ◆ Varactors
- Breakdown Region
  - ◆ Zener Diodes
- Photodiodes and Solar Cells
- Light-Emitting Diodes