

**DUBLIN INSTITUTE OF TECHNOLOGY
KEVIN STREET, DUBLIN 8**

**Diploma in Electronic
Engineering**
YEAR 3

AUTUMN EXAMINATION 2000

ELECTRIC CIRCUITS AND SIGNAL PROCESSING

MR. P. Tobin

MR. K. Tiernan

MR. C. Bruce

DATE:

Attempt three questions

Smith chart

Laplace tables

Butterworth and Chebychev tables

$c = 3 \cdot 10^8$ m/s

1. (a) Obtain a transfer function for a third-order high-pass filter, which uses a Butterworth loss function, and which meets the following specification:

The maximum passband loss $A_{max} = 3$ dB

The minimum stopband loss $A_{min} = 28$ dB

The passband edge frequency $\omega_p = 6000$ rs^{-1}

The stopband edge frequency $\omega_s = 2000$ rs^{-1}

[10 marks]

- (b) A second-order IGMF bandpass active filter is shown in Figure 1. Show, by means of nodal analysis, how the transfer function is:

$$-\frac{s \frac{1}{R_1 C}}{s^2 + s \frac{2}{CR_2} + \frac{1}{C^2 R_1 R_2}} = \frac{V_{out}}{V_{in}}$$

[8 marks]

Calculate a value for the centre frequency ω_0 , the -3 dB bandwidth and the passband gain for the circuit values given.

$R_1 = 1$ k Ω , $R_2 = 100$ k Ω , $C = 15$ nF.

[7 marks]

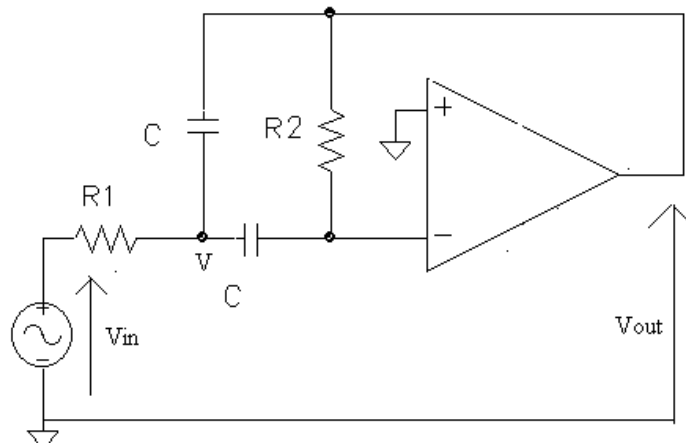


Figure 1

- 2.(a) (a) Discuss the effect, component tolerance, has on the performance of active filters.

[5 marks]

- (b) The frequency spectrum of a 1 kHz squarewave is shown in figure 2. It is desired to extract, from this squarewave, a 1 kHz sinusoidal signal. Obtain a transfer function for a low-pass filter, which will produce a maximum attenuation of the fundamental component of 1 dB. The third harmonic (3 kHz) should be attenuated by 12 dB (Butterworth loss functions tables are available for use in your analysis).

[12 marks]

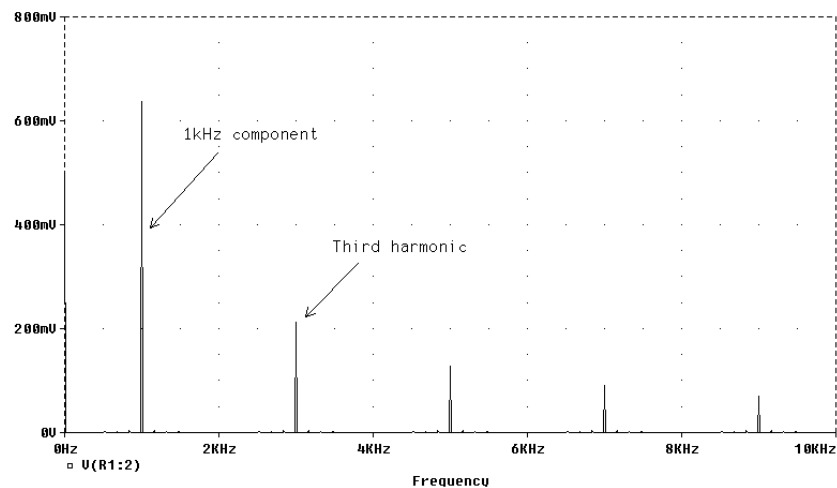


Figure 2

- (c) Show how you could implement the transfer function obtained in part (a) using a Sallen and Key VCVS active filter. [8 marks]
- 3 (a) Define the term voltage reflection coefficient. Use the solution for the voltage along a transmission line $V = V_1 e^{-(\alpha + j\beta)z} + V_2 e^{(\alpha + j\beta)z}$ in your answer. [7 marks]
- (b) A transmission line with characteristic impedance Z_o equal to 75Ω , is terminated in an impedance $Z_L = 40 + j20 \Omega$. Calculate
- The reflection coefficient,
 - The voltage standing ratio, and
 - The input impedance.
- [6 marks]
- (c) Hence use a Smith chart to verify approximately, the three values calculated in (i) to (iii). [12 marks]