


EE 380-1, Control Engineering - I, Quiz# 3

Form-A

Saturday, March 22nd, 2004, Dr. Ahmad A. Masoud

Name:

Student Number:

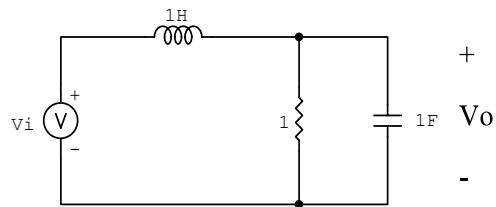

Write the state space equations for the above circuit and use them to derive its transfer function.