

Factor Form

□ Factor forms – beyond SOP

- Example:
 $(ad + b'c)(c + d'(e + ac')) + (d + e)fg$

□ Advantages

- good representation reflecting logic complexity (SOP may not be representative)
 - E.g., $f = ad + ae + bd + be + cd + ce$ has complement in simpler SOP $f' = a'b'c' + d'e'$; effectively has simple factor form $f = (a + b + c)(d + e)$
- in many design styles (e.g. complex gate CMOS design) the implementation of a function corresponds directly to its factored form
- good estimator of logic implementation complexity
- doesn't blow up easily

□ Disadvantages


- not as many algorithms available for manipulation

53

Factor Form

□ Factored forms are useful in **estimating** area and delay in multi-level logic

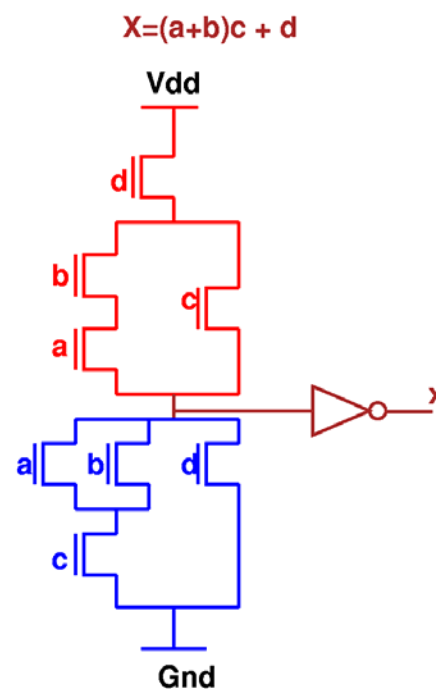- Note: literal count \approx transistor count \approx area
 - however, area also depends on wiring, gate size, etc.
 - therefore very crude measure



54

Factor Form

- There are functions whose sizes are **exponential** in the SOP representation, but **polynomial** in the factored form

- **Example**

Achilles' heel function

$$\prod_{i=1}^{i=n/2} (x_{2i-1} + x_{2i})$$


There are n literals in the factored form and $(n/2) \times 2^{n/2}$ literals in the SOP form.

55

Factor Form

- Factored forms can be graphically represented as labeled **trees**, called **factoring trees**, in which each internal node including the root is labeled with either $+$ or \times , and each leaf has a label of either a variable or its complement

 - **Example:** factoring tree of $((a'+b)cd+e)(a+b')+e'$



56

Multi-Level Logic Minimization

- Basic techniques in Boolean network manipulation:
 - structural manipulation (change network topology)
 - node simplification (change node functions)
 - node minimization using don't cares

57

Multi-Level Logic Minimization Structural Manipulation

Restructuring Problem: Given initial network, find **best** network.

Example:

$$f_1 = abcd + abce + ab'cd' + ab'c'd' + a'c + cdf + abc'd'e' + ab'c'df'$$

$$f_2 = bdg + b'dfg + b'd'g + bd'eg$$

minimizing,

$$f_1 = bcd + bce + b'd' + a'c + cdf + abc'd'e' + ab'c'df'$$

$$f_2 = bdg + dfg + b'd'g + d'eg$$

factoring,

$$f_1 = c(b(d+e) + b'(d'+f) + a') + ac'(bd'e' + b'df')$$

$$f_2 = g(d(b+f) + d'(b'+e))$$

decompose,

$$f_1 = c(b(d+e) + b'(d'+f) + a') + ac'x'$$

$$f_2 = gx$$

$$x = d(b+f) + d'(b'+e)$$

Two problems:

- find good **common** subfunctions
- effect the **division**

58

Multi-Level Logic Minimization

Structural Manipulation

Basic operations:

1. Decomposition (for a single function)

$$f = abc + abd + a'c'd' + b'c'd'$$

↓

$$f = xy + x'y' \quad x = ab \quad y = c + d$$

2. Extraction (for multiple functions)

$$f = (az + bz')cd + e \quad g = (az + bz')e' \quad h = cde$$

↓

$$f = xy + e \quad g = xe' \quad h = ye \quad x = az + bz' \quad y = cd$$

3. Factoring (series-parallel decomposition)

$$f = ac + ad + bc + bd + e$$

↓

$$f = (a + b)(c + d) + e$$

59

Multi-Level Logic Minimization

Structural Manipulation

Basic operations (cont'd):

4. Substitution

$$f = a + bc \quad g = a + b$$

↓

$$f = g(a + c) \quad g = a + b$$

5. Collapsing (also called elimination)

$$f = ga + g'b \quad g = c + d$$

↓

$$f = ac + ad + bc'd' \quad g = c + d$$


Note: “division” plays a key role in all these operations

60

Multi-Level Logic Minimization

Node Simplification

 - Goal: For any node of a given Boolean network, find a **least-cost** SOP expression among the set of permissible functions for the node
 - Don't care computation + two-level logic minimization




combinational Boolean network

61

Combinational Logic Minimization

- **Two-level:** minimize # product terms and # literals
 - E.g., $F = x_1'x_2'x_3' + x_1'x_2'x_3 + x_1x_2'x_3' + x_1x_2'x_3 + x_1x_2x_3' \Rightarrow F = x_2' + x_1x_3'$
- **Multi-level:** minimize the # literals (**area** minimization)
 - E.g., equations are optimized using a smaller number of literals
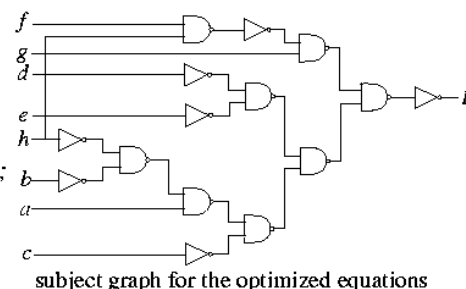
$$\begin{array}{l}
 t1 = a + b \ c; \\
 t2 = d + e; \\
 t3 = a \ b + d; \\
 t4 = t1 \ t2 + fg; \\
 t5 = t4 \ h + t2 \ t3; \\
 F = t5';
 \end{array}
 \xrightarrow{\text{logic optimization}}
 \begin{array}{l}
 t1 = d + e; \\
 t2 = b + h; \\
 t3 = a \ t2 + c; \\
 t4 = t1 \ t3 + fg \ h;
 \end{array}$$



subject graph for the optimized equations


62

Timing Analysis and Optimization

□ Delay model at logic level

■ Gate delay model (our focus)

 - Constant gate delay, or pin-to-pin gate delay
- Not accurate



■ Fanout delay model

- Gate delay considering fanout load (# fanouts)
- Slightly more accurate

■ Library delay model

- Tabular delay data given in the cell library
 - Determine delay from **input slew** and **output load**
 - Table look-up + interpolation/extrapolation
- Accurate

63


Timing Analysis and Optimization

Gate Delay

The delay of a gate depends on:

 
1. Output Load

- Capacitive loading \propto charge needed to swing the output voltage
- Due to interconnect and logic fanout



 2. Input Slew

- Slew = transition time
- Slower transistor switching \Rightarrow longer delay and longer output slew




64

Timing Analysis and Optimization

Timing Library

 - Timing library contains all relevant information about each standard cell
 - E.g., pin direction, clock, pin capacitance, etc.
- Delay (fastest, slowest, and often typical) and output slew are encoded for each input-to-output path and each pair of transition directions
- Values typically represented as 2 dimensional look-up tables (of output load and input slew)
 - Interpolation is used



```
Path(
    inputPorts(A),
    outputPorts(Z),
    inputTransition(01),
    outputTransition(10),
    "delay_table_1",
    "output_slew_table_1"
);
```


“delay_table_1”
Output load (nF)

	1.0	2.0	4.0	10.0
0.1	2.1	2.6	3.4	6.1
0.5	2.4	2.9	3.9	7.2
1.0	2.6	3.4	4.0	8.1
2.0	2.8	3.7	4.9	10.3

Input slew (ns)

Static Timing Analysis

 - **Arrival time:** the time signal arrives
 - Calculated from input to output in the topological order
- **Required time:** the time signal must ready (e.g., due to the clock cycle constraint)
 - Calculated from output to input in the reverse topological order
- **Slack** = required time – arrival time
 - Timing flexibility margin (positive: good; negative: bad)



$A(j)$: arrival time of signal j
 $R(k)$: required time or for signal k
 $S(k)$: slack of signal k
 $D(j,k)$: delay of node j from input k

$$A(j) = \max_{k \in FI(j)} [A(k) + D(j,k)]$$


$$r(j,k) = R(j) - D(j,k)$$

$$R(k) = \min_{j \in FO(k)} [r(j,k)]$$

$$S(k) = R(k) - A(k)$$

Static Timing Analysis

 - Arrival times known at I_1 and I_2
- Required times known at I_3 , I_4 , and I_5
- Delay analysis gives arrival and required times (hence slacks) for combinational blocks C_1 , C_2 , C_3 , C_4



67


Static Timing Analysis

- **Arrival time** can be computed in the **topological order from inputs to outputs**
 - When a node is visited, its output arrival time is:
the max of its fanin arrival times + its own gate delay
- **Required time** can be computed in the **reverse topological order from outputs to inputs**
 - When a node is visited, its input required time is:
the min of its fanout required times – its own gate delay

68

Static Timing Analysis

Example

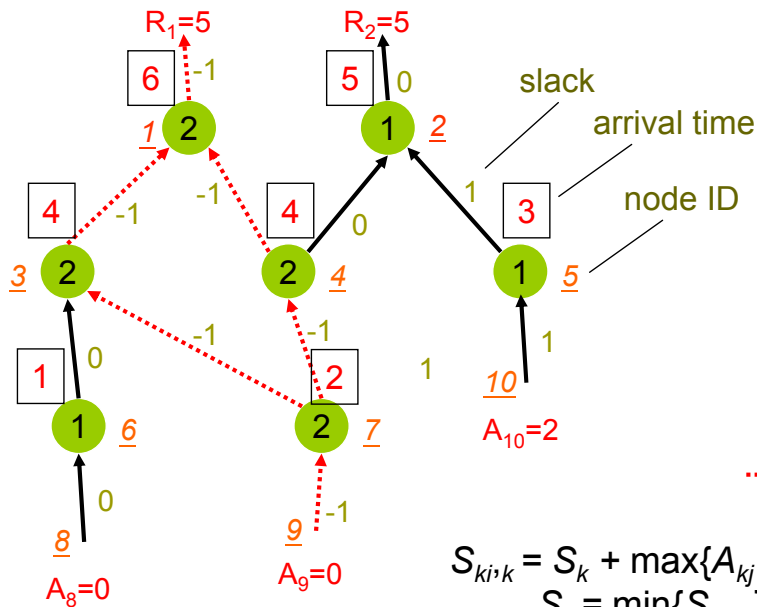

$$A_1 = 6 \quad R_1 = 5$$

$$A_2 = 5 \quad R_2 = 5$$

$$S_1 = -1 \quad R_3 = 3$$

$$S_2 = 0 \quad R_7 = 1$$

$$S_{3,1} = -1 \quad R_9 = -1$$

$$S_{4,1} = -1$$

$$S_{4,2} = 0$$

$$S_{5,2} = 1$$

$$S_{6,3} = 0$$

$$S_{7,3} = -1$$

$$S_{7,4} = -1$$

$$S_{7,5} = 1$$

$$S_{8,6} = 0$$

$$S_{9,7} = -1$$

..... critical path edges

$$S_{k_i \rightarrow k} = S_k + \max\{A_{k_j}\} - A_{k_i}, k_j, k_i \in \text{fanin}(k)$$

$$S_k = \min\{S_{k \rightarrow k_j}\}, k_j \in \text{fanout}(k)$$

69

Timing Optimization


- Identify timing critical regions
- Perform timing optimization on the selected regions
 - E.g., gate sizing, buffer insertion, fanout optimization, tree height reduction, etc.

70

Timing Optimization

□ Buffer insertion

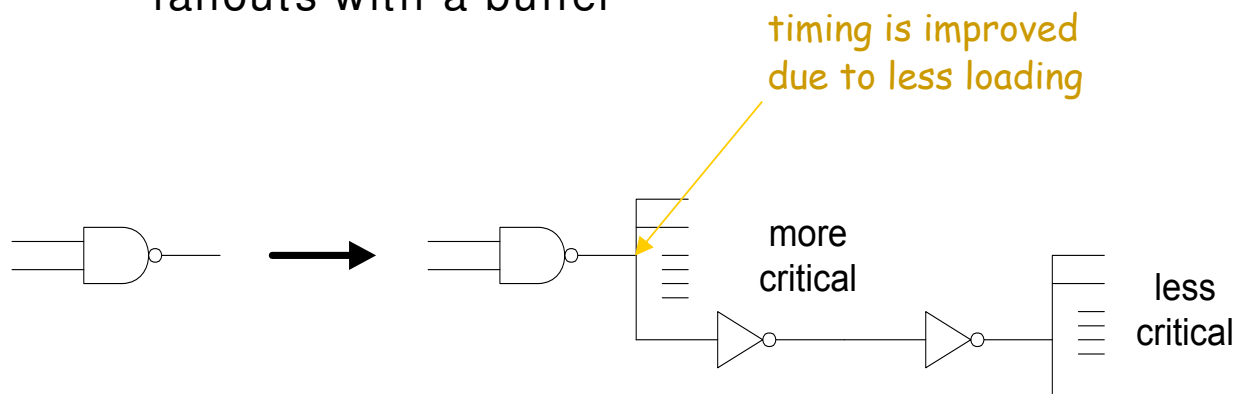- Divide the fanouts of a gate into critical and non-critical parts, and drive the non-critical fanouts with a buffer




71

Timing Optimization

□ Fanout optimization

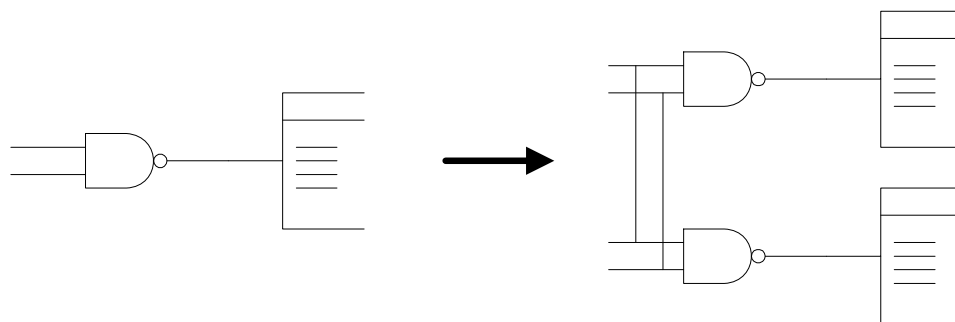
- Split the fanouts of a gate into several parts. Each part is driven by a copy of the original gate.



72

Timing Optimization


Tree height reduction

 

73

Timing Optimization


Tree height reduction

 

74

Combinational Optimization

□ From Boolean functions to circuits

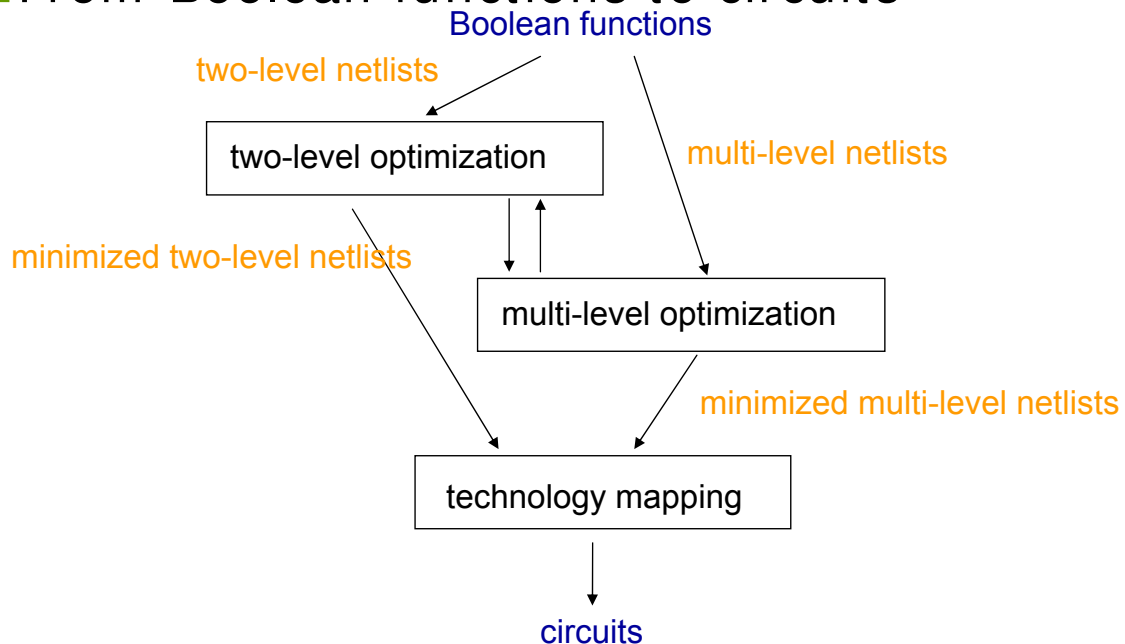


75

Technology Independent vs. Dependent Optimization

- Technology independent optimization produces a two-level or multi-level netlist where literal and/or cube counts are minimized
- Given the optimized netlist, its logic gates are to be implemented with library cells
- The process of associating logic gates with library cells is **technology mapping**
 - Translation of a technology independent representation (e.g. Boolean networks) of a circuit into a circuit for a given technology (e.g. standard cells) with optimal cost

76


Technology Mapping

 

- **Standard-cell technology mapping:** standard cell design
 - Map a function to a limited set of pre-designed library cells
- **FPGA technology mapping**
 - Lookup table (LUT) architecture:
 - E.g., Lucent, Xilinx FPGAs
 - Each lookup table (LUT) can implement all logic functions with up to k inputs ($k = 4, 5, 6$)
 - Multiplexer-based technology mapping:
 - E.g., Actel FPGA
 - Logic modules are constructed with multiplexers

77

Standard-Cell Based Design

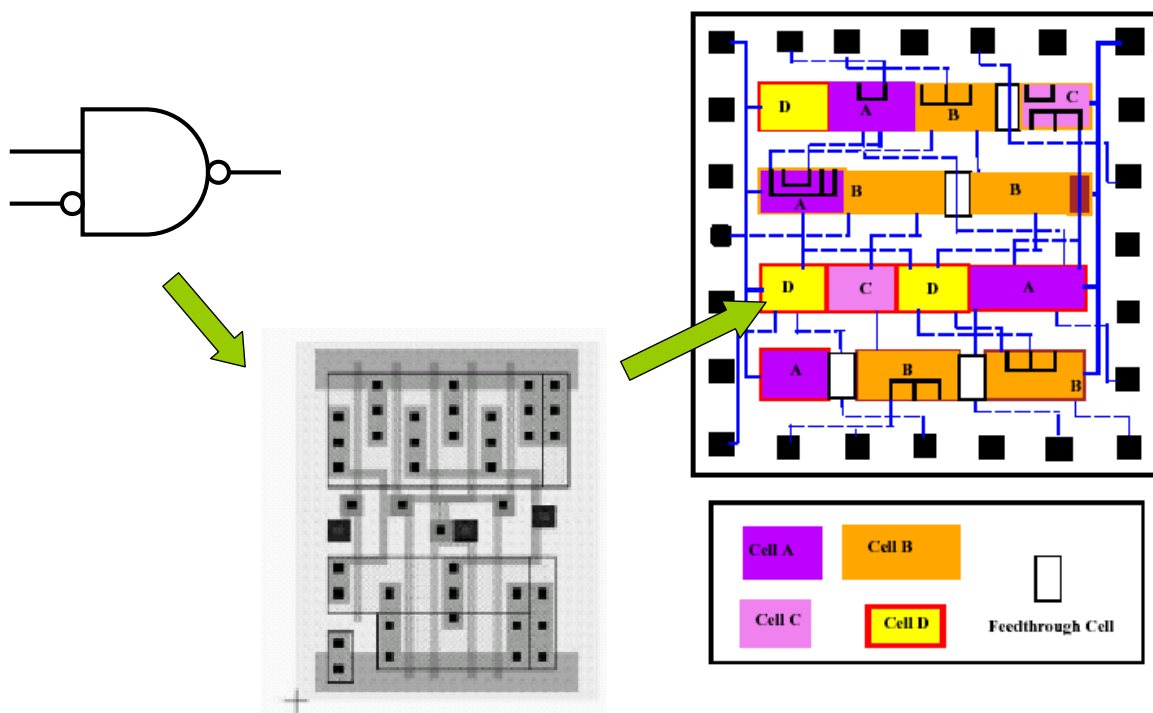

78

Technology Mapping

□ Formulation:

- Choose base functions
 - Ex: 2-input NAND and Inverter
- Represent the (optimized) Boolean network with base functions
 - Subject graph
- Represent library cells with base functions
 - Pattern graph
 - Each pattern is associated with a cost depending on the optimization criteria, e.g., area, timing, power, etc.

□ Goal:

- Find a minimal cost covering of a subject graph using pattern graphs

79

Technology Mapping

□ **Technology Mapping:** The optimization problem of finding a minimum cost covering of the subject graph by choosing from a collection of pattern graphs of gates in the library.

□ A **cover** is a collection of pattern graphs such that every node of the subject graph is contained in one (or more) of the pattern graphs.

□ The cover is further constrained so that each input required by a pattern graph is actually an output of some other pattern graph.


80

Technology Mapping

 Example

Subject graph

$$\begin{aligned}
 t1 &= d + e \\
 t2 &= b + h \\
 t3 &= a t2 + c \\
 t4 &= t1 t3 + f g h \\
 F &= t4'
 \end{aligned}$$




81

Technology Mapping

Example

Pattern graphs (1/3)






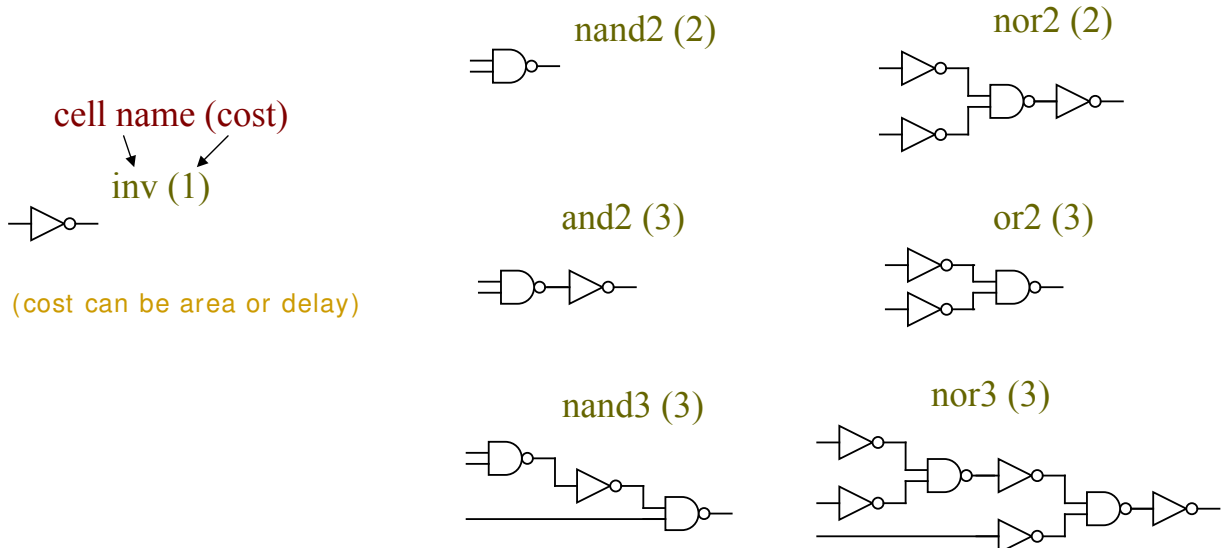


82

Technology Mapping

Example

Pattern graphs (2/3)

   
 
 
 


83

Technology Mapping

Example

Pattern graphs (3/3)

    

84

Technology Mapping


Example

A trivial covering

Mapped into NAND2's and INV's

- 8 NAND2's and 7 INV's at cost of 23
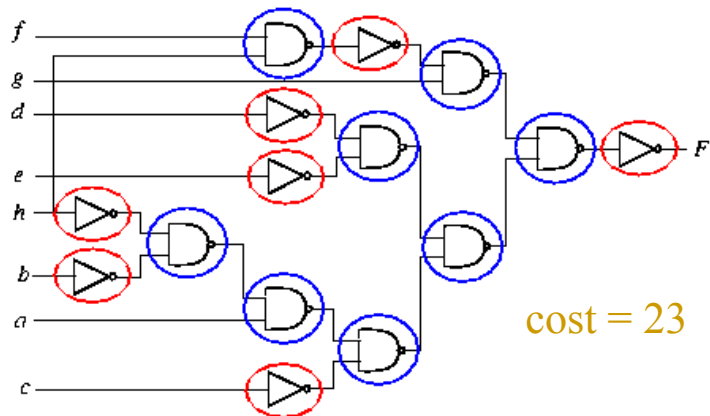
$$\begin{aligned}
 t1 &= d + e; \\
 t2 &= b + h; \\
 t3 &= a \ t2 + c; \\
 t4 &= t1 \ t3 + f \ g \ h;
 \end{aligned}$$




85

Technology Mapping

Example

A better covering

 


For a covering to be legal, every input of a pattern graph must be the output of another pattern graph!

86

Technology Mapping

□ Example

- An even better covering

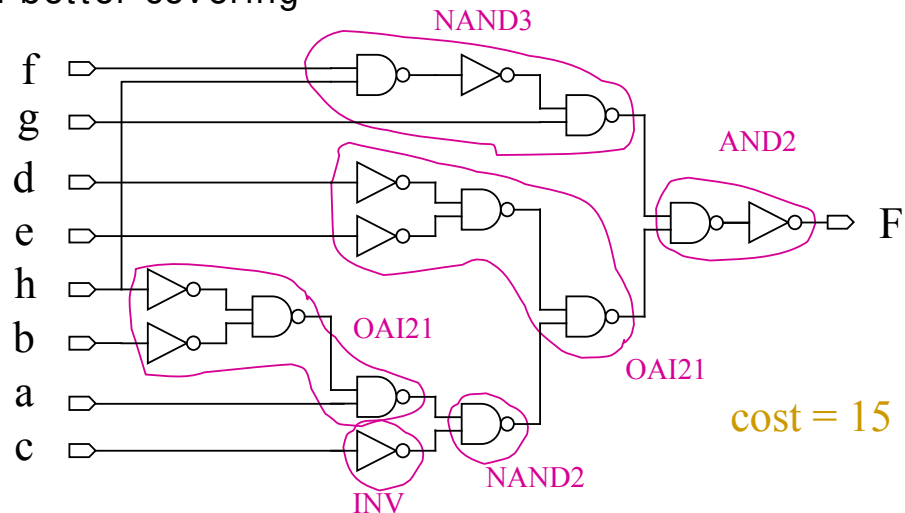

For a covering to be legal, every input of a pattern graph must be the output of another pattern graph!

87

Technology Mapping


□ Complexity of covering on directed acyclic graphs (DAGs)

- NP-complete
- If the subject graph and pattern graphs are trees, then an efficient algorithm exists (based on [dynamic programming](#))

88

Technology Mapping DAGON Approach

 
- Partition a subject graph into trees
 - Cut the graph at all multiple fanout points
- Optimally cover each tree using dynamic programming approach
- Piece the tree-covers into a cover for the subject graph



89

Technology Mapping DAGON Approach

 - Principle of optimality: optimal cover for the tree consists of a match at the root plus the optimal cover for the sub-tree starting at each input of the match




$$C(\text{root}) = m + C(I_1) + C(I_2) + C(I_3) + C(I_4)$$

cost of a leaf (i.e. primary input) = 0

90

Technology Mapping DAGON Approach

Example Library

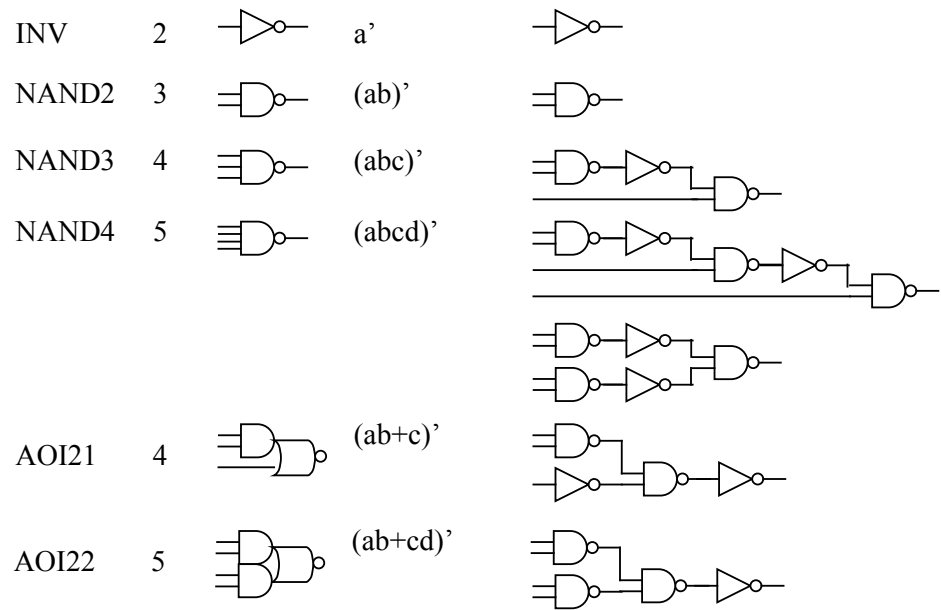


library element

base-function representation

Technology Mapping DAGON Approach

Example

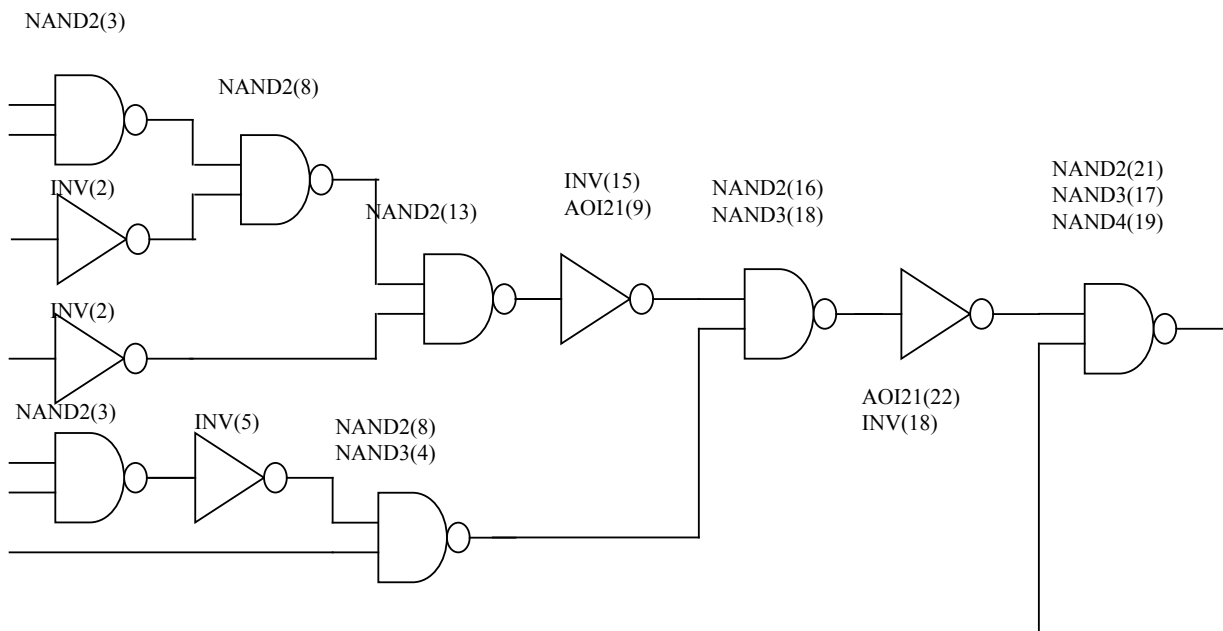

Technology Mapping

DAGON Approach

- Complexity of DAGON for tree mapping is controlled by finding **all** sub-trees of the subject graph isomorphic to pattern trees
- **Linear** complexity in both the size of subject tree and the size of the collection of pattern trees
 - Consider library size as constant

93

Technology Mapping

DAGON Approach

- Pros:
 - Strong algorithmic foundation
 - Linear time complexity
 - Efficient approximation to graph-covering problem
 - Give locally optimal matches in terms of both area and delay cost functions
 - Easily “portable” to new technologies
- Cons:
 - With only a local (to the tree) notion of timing
 - Taking load values into account can improve the results
 - Can destroy structures of optimized networks
 - Not desirable for well-structured circuits
 - Inability to handle non-tree library elements (XOR/XNOR)
 - Poor inverter allocation


94

Technology Mapping


DAGON Approach

□ DAGON can be improved by

 - Adding a pair of inverters for each wire in the subject graph
- Adding a pattern of a wire that matches two inverters with zero cost



2 INV
1 AIO21

 

2 NOR2

95

Available Logic Synthesis Tools

□ Academic CAD tools:

- Espresso (heuristic two-level minimization, 1980s)
- MIS (multi-level logic minimization, 1980s)
- SIS (sequential logic minimization, 1990s)
- ABC (sequential synthesis and verification system, 2005-)

□ <http://www.eecs.berkeley.edu/~alanmi/abc/>

96