

**DUBLIN INSTITUTE OF TECHNOLOGY  
KEVIN STREET, DUBLIN 8**

---

**Diploma in Electronic  
Engineering**  
YEAR 3

---

**Winter EXAMINATION 2000**

---

**ELECTRIC CIRCUITS AND SIGNAL PROCESSING**

MR. P. Tobin

MR. K. Tiernan

MR. C. Bruce

DATE:

Attempt three questions

Smith chart

Laplace tables

Chebychev tables

$c=3.10^8$  m/s

1. (a) A low-pass filter is required to meet the filter specification:

The maximum passband loss  $A_{max} = 0.5$  dB

The minimum stopband loss  $A_{min} = 12$  dB

The passband edge frequency  $\omega_p = 100$   $\text{rs}^{-1}$

The stopband edge frequency  $\omega_s = 400$   $\text{rs}^{-1}$

Determine the filter order  $n$  using the relationship

$$n = \frac{\log_{10} \left[ \frac{10^{0.1A_{min}} - 1}{10^{0.1A_{max}} - 1} \right]}{2 \log_{10} \left( \frac{\omega_s}{\omega_p} \right)}$$

Sketch the pole-zero diagram using the relationship between  $n$  and the angle  $\theta_k$ , between the poles

$$\theta_k = \frac{360^\circ}{2n}$$

Hence obtain a transfer function, which meets the specification.

Note: Butterworth tables are not supplied.

[15 marks]

(b) Obtain circuit values for a Sallen and Key VCVS circuit configuration that would meet the specification in part (a).

[10 marks]

2.(a) State one advantage and one disadvantage of using Chebychev polynomials in approximation loss function analysis.

[5 marks]

(b) A bandpass filter is required for a particular application, which will tolerate ripple in the passband equal to 0.5 dB. The specification for the bandpass filter is:

$\omega_{bs1}$  = the lower stopband edge frequency = 688  $\text{rs}^{-1}$

$\omega_{bs2}$  = the upper stopband edge frequency = 1930  $\text{rs}^{-1}$

$\omega_{bp1}$  = the lower passband edge frequency = 970  $\text{rs}^{-1}$

$\omega_{bp2}$  = the upper passband edge frequency = 1370  $\text{rs}^{-1}$

The maximum passband attenuation  $A_{max} = 0.5$  dB.

The minimum stopband attenuation  $A_{min} = 15$  dB.

Obtain the bandpass transfer function, which will meet this specification. (Use the available Chebychev tables).

[20 marks]

3.(a) Define the following transmission line terms: Voltage standing wave ratio and voltage reflection coefficient.

[5 marks]

(b) A transmission line, whose characteristic impedance  $Z_o = 300 + j0$   $\Omega$ , has an antenna of impedance  $225 - j175$   $\Omega$  connected as a load. Matching by means of a single stub connected, at a distance  $d$  metres from the load, is used. Estimate the length in metres of the stub and the distance  $d$  if the operating frequency  $f = 500$  MHz. Assume that the stub is formed from a section of the same air-spaced transmission line.

[12 marks]

(c) Calculate the characteristic impedance, phase coefficient and attenuation constant for a 10 km length of telephone cable, operating at a frequency of 10 kHz, if the cable has the following, primary transmission line parameters:

$L = 700$  mH per km,  $C = 0.05$   $\mu$ F per km,  $R = 28$   $\Omega$  per km,  $G = 1$   $\mu$ S per km  
[8 marks]