

**DUBLIN INSTITUTE OF TECHNOLOGY
KEVIN STREET, DUBLIN 8**

**Diploma in Electronic
Engineering**
YEAR 3

AUTUMN EXAMINATIONS 1999

ELECTRIC CIRCUITS AND SIGNAL PROCESSING

MR. P. Tobin

MR. K. Tiernan

MR. C. Bruce

DATE:

Attempt three questions

Smith chart

Laplace tables

Butterworth and Chebychev tables

- 1.(a) Obtain a transfer function for a high-pass filter, which uses a Butterworth loss function, and which meets the following specification:

The maximum passband loss $A_{max} = 3$ dB

The minimum stopband loss $A_{min} = 28$ dB

The passband edge frequency $\omega_p = 6000$ rs^{-1}

The stopband edge frequency $\omega_s = 2000$ rs^{-1}

[10 marks]

- (b) Show how the transfer function, for the second stage of the Sallen and Key, high-pass filter shown in figure 1, is:

$$\frac{E_3}{E_2} = \frac{s^2}{s^2 + s \frac{2}{CR_2} + \frac{1}{C^2 R_1 R_2}}$$

[8 marks]

Hence calculate component values for this circuit, which could implement the transfer function obtained in part (a).

$R = 20$ k Ω .

[7 marks]

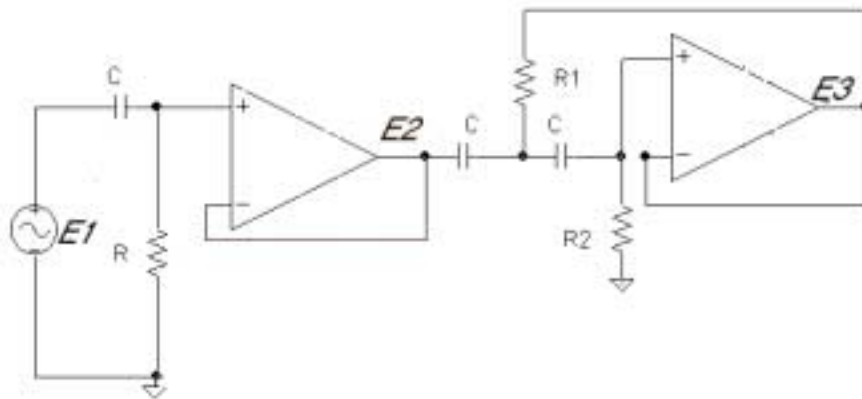


Figure 1

- 2.(a) It is desired to produce a 1 kHz sinusoidal signal from a 1 kHz squarewave. Obtain the transfer function for a low-pass filter, which will produce a maximum attenuation of the fundamental signal of 1 dB. The third harmonic (3 kHz) should be attenuated by 12 dB (Butterworth loss functions tables are available for use in your analysis).

[12 marks]

- (b) Identify the circuit shown in figure 2. State one possible application for this circuit. Obtain the high-pass transfer function, assuming equal value resistances.

[13 marks]

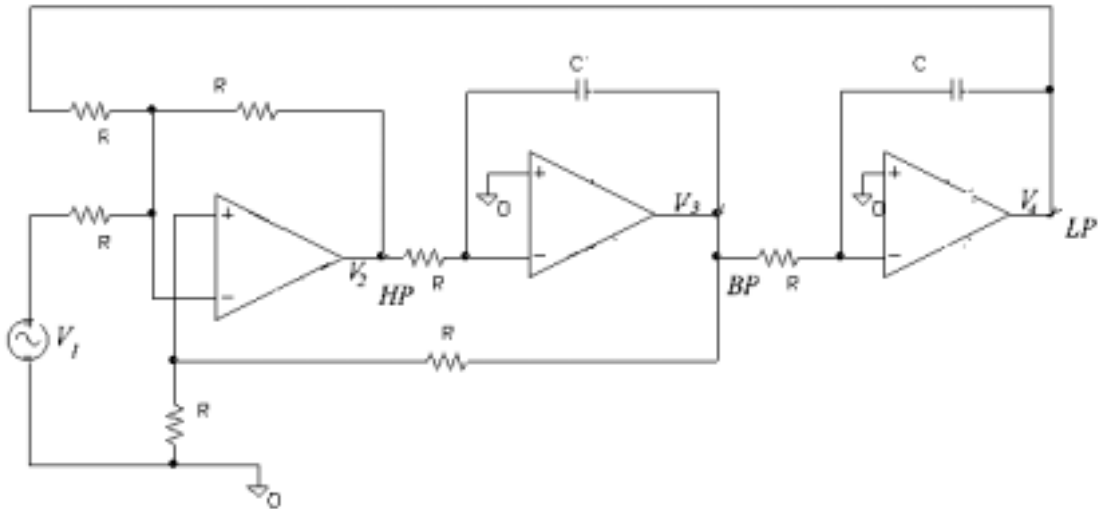


Figure 2

- 3 (a) A 10 km length of screened telephone cable, operating at a frequency of 10 kHz, has the following, primary transmission line parameters:

$$L = 700 \text{ mH per km,}$$

$$C = 0.05 \text{ } \mu\text{F per km,}$$

$$R = 28 \text{ } \Omega \text{ per km, and}$$

$$G = 1 \text{ } \mu\text{S per km}$$

Determine the phase and attenuation constants for this cable and hence calculate the characteristic impedance.

[8 marks]

- (b) An expression for the input impedance of a transmission line, terminated in a resistance $Z_R = 35 \text{ } \Omega$ is:

$$Z_{in} = Z_o \left[\frac{\frac{Z_R}{\tan \beta \ell} + jZ_o}{\frac{Z_o}{\tan \beta \ell} + jZ_R} \right]$$

Where β is the phase change coefficient and Z_o is the characteristic impedance equal to $75 \text{ } \Omega$. Determine the input impedance of a section of line whose length is $\lambda/4$ metres.

[7 marks]

- (c) Describe one graphical technique for matching a transmission line to a load. Illustrate your answer using a Smith chart.

[10 marks]